

CIRCUIT:

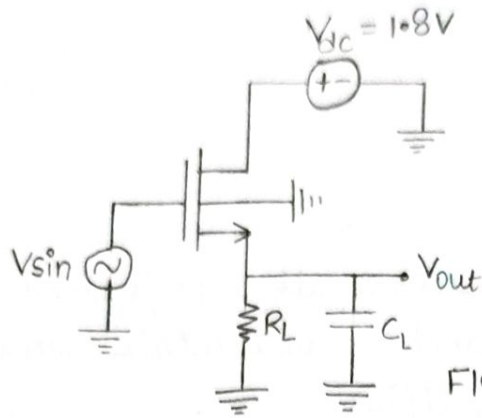


FIG: SOURCE FOLLOWER AMPLIFIER

SIMULATIONS:

PARAMETRIC ANALYSIS:

| Sweep | 0 | 0.3 | 0.6 | 0.9 | 1.2 | 1.5 | 1.8 |
|-----------|-----------|-------------|-------------|--------------|--------------|-------------|--------------|
| Region | 0 | 3 | 3 | 2 | 2 | 2 | 2 |
| R_{out} | 64.35 G | 7.78 M | 206.49 K | 78.37 K | 45.03 K | 29.99 K | 21.26 K |
| I_D | 30.25 p | 266.3 n | 12.05 μ | 32.93 μ | 36.0 μ | 89.09 μ | 104.75 μ |
| g_m | 951.71 p | 7.422 μ | 236.2 μ | 529.15 μ | 770.82 μ | 963.8 μ | 1.113 m |
| V_{th} | 0.473 | 0.4733 | 0.479 | 0.534 | 0.569 | 0.599 | 0.627 |
| V_{ds} | 1.8 | 1.797 | 1.679 | 1.470 | 1.239 | 0.999 | 0.752 |
| V_{gs} | -320.58 n | 0.297 | 0.479 | 0.570 | 0.639 | 0.699 | 0.752 |

• DC ANALYSIS: Transistor operating in Region 2.


• TRANSIENT ANALYSIS: $V_{in pp} = 2 \text{ mV}$ $V_{out pp} = 1.55 \text{ mV}$
 $A_v = 0.775$

• AC ANALYSIS: Gain vs freq. and phase vs freq. graphs are plotted.

$$\text{Gain} = -2.17099 \text{ dB} \Rightarrow \text{Gain} = 0.778$$

File Name: 17-12-2018

Transient response of the first

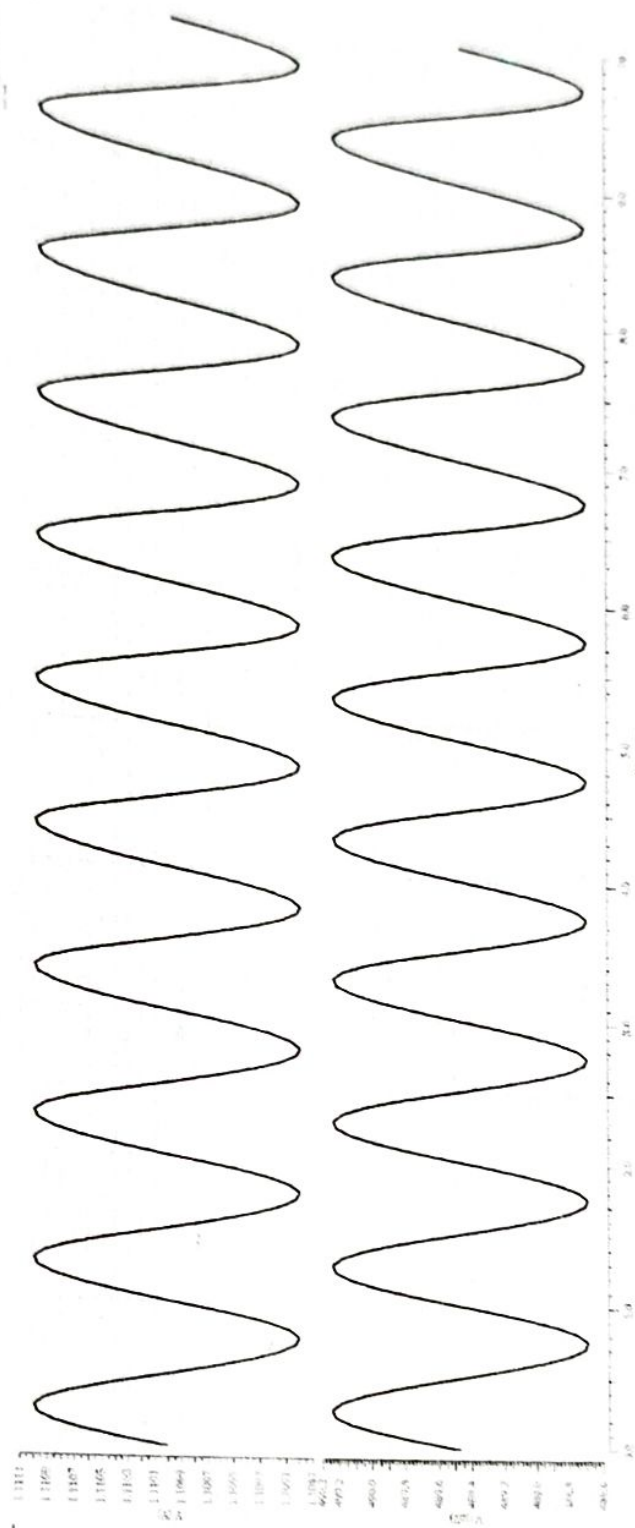


Transient response of source follower

Experiment No. 7

Aim: Simulation and analysis of source follower circuit.

Tool: PSpice

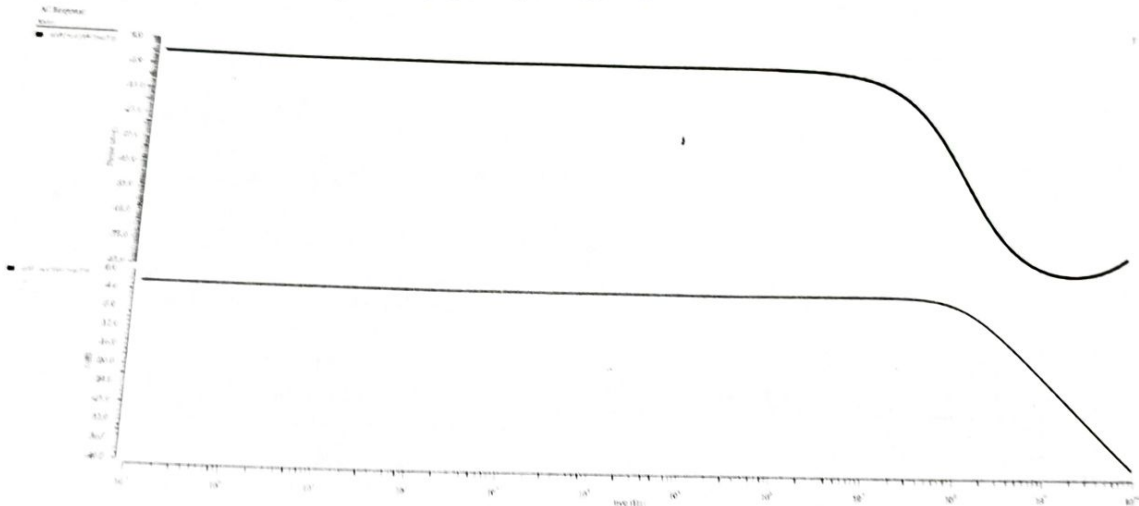

gain Vs freq and phase Vs freq of source follower

$$50\mu = \frac{300\mu}{2} \times \frac{8100}{3} (V_{gs} - V_{th})^2$$

$$\Rightarrow V_{gs} - V_{th} = 0.11$$

$$\therefore V_{gs} = V_{in} - V_{out}$$

$$\therefore \underline{V_{in} = 1.1V}$$

$$\Rightarrow \frac{W}{L} = \frac{(1m)^2 (0.9m)^2}{2 \times 300\mu \times 50\mu}$$

$$\text{for } \Rightarrow L = 0.18\mu m$$

$$\underline{W = 4.86\mu m}$$

Result: We have successfully performed DC, AC, transient and parametric analysis of source follower amplifier.

